

**ANURAG Engineering College**  
(An Autonomous Institution)

II B.Tech. I Semester Supplementary Examinations, December – 2024

**ELECTRICAL CIRCUIT ANALYSIS**  
(ELECTRICAL AND ELECTRONICS ENGINEERING)

**Time: 3 Hours**

**Max. Marks: 75**

**Section – A (Short Answer type questions)**

**(25 Marks)**

**Answer All Questions**

1. What are the uses of source transformation?
2. State compensation theorem.
3. Derive transient response for R-L circuit using AC excitation
4. Find Laplace transform of  $f(t) = \cos 2t + e^{-3t}$ ,  $t > 0$
5. Write the circle equation of RL circuit with R variable.
6. A series circuit has  $R=4$  ohms,  $L=25$  mH, and  $C=150$   $\mu$ F. What is the bandwidth?
7. Derive expressions for transmission parameters of two two-port networks connected in cascade.
8. Derive the expression for Y parameters in terms of ABCD parameters.
9. What are the properties of tie-set matrix?
10. Define the following terms  
i) Graph    ii) Link    iii) Tree


Course Outcome	B.T Level	Marks
CO1	L1	2M
CO1	L1	3M
CO2	L2	2M
CO2	L2	3M
CO3	L2	2M
CO3	L2	3M
CO4	L2	2M
CO4	L2	3M
CO5	L1	2M
CO5	L2	3M

**Section B (Essay Questions)**

**Answer all questions, each question carries equal marks.**

**(5 X 10M = 50M)**

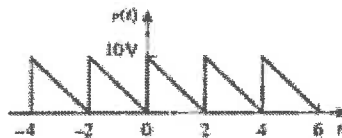
11. A) i) State and explain Maximum power transfer theorem.  
ii) For the periodic wave form shown in the following figure, determine average and rms value, form factor.



**OR**

- B) i) Describe Ideal current source and Ideal voltage sources with examples.  
ii) Determine the current  $I_o$  in 1 Ohm resistor of the circuit shown in figure.

CO1	L2	4M
CO1	L3	6M

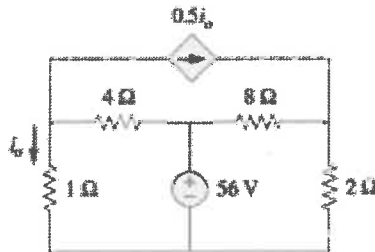

12. A) i) Determine the transient current through a series R-C circuit when it is connected to a sinusoidal voltage source.  
ii) In a series RLC circuit,  $R=6$  ohms,  $L=2$  H,  $C=2$  F. A DC voltage of 50 V is applied at  $t=0$ . Obtain the expression for  $i(t)$  using differential equation approach.


CO2	L2	5M
CO2	L3	5M

**OR**

- |  |     |    |     |
|--|-----|----|-----|
| <p>B) In a series RLC circuit <math>L=0.3</math> H, and <math>C=4</math> F. A DC voltage of 50 V is applied at <math>t=0</math>. Obtain an expression for current <math>i(t)</math> in the circuit, when (i) <math>R= 5 \Omega</math> (ii) <math>R= 6 \Omega</math>.</p> | CO2 | L3 | 10M |
| <p>13. A) i) Illustrate the concept of resonance.<br/>ii) A series RLC circuit has the following parameter values <math>R= 10\Omega</math>, <math>L=0.01</math> H and <math>C= 10 \mu\text{F}</math>. Find the Q factor of the circuit at resonance.</p>                 | CO3 | L2 | 4M  |
|  | CO3 | L3 | 6M  |


**OR**

- |  |     |    |     |
|--|-----|----|-----|
| <p>B) A voltage of <math>V = 270\angle 0^\circ</math> V is applied to a series circuit of fixed resistance <math>R = 8</math> ohms and a variable capacitance C. Sketch the admittance and current locus diagrams.</p> | CO3 | L3 | 10M |
| <p>14. A) i) Classify filters in detail.<br/>ii) For the following network shown in below Figure. Determine h-parameters.</p>  | CO4 | L2 | 4M  |
|  | CO4 | L3 | 6M  |

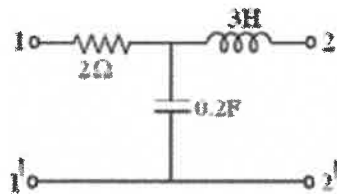


**OR**

- |  |     |    |     |
|--|-----|----|-----|
| <p>B) For the two port network given below, Determine Y and ABCD parameters.</p> | CO4 | L3 | 10M |
|--|-----|----|-----|

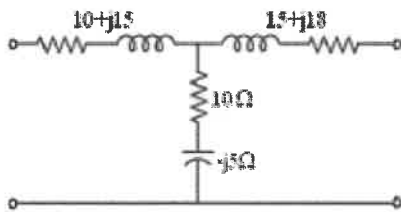

- |   |     |    |    |
|---|-----|----|----|
| <p>15. A) i) Explain the measurement of power in a balanced 3-phase system using a single watt meter.<br/>ii) For the network shown in figure, obtain the oriented graph of the network. Write the cut-set matrix of the graph and determine the loop currents. All the values of resistances in the circuit are in ohms.</p> | CO5 | L2 | 4M |
|   | CO5 | L3 | 6M |

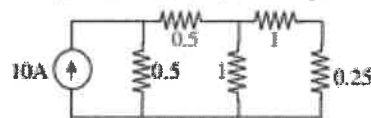

**OR**

- |   |     |    |     |
|---|-----|----|-----|
| <p>B) For the network shown in figure 3(a) draw the graph and show some possible trees.</p> | CO5 | L3 | 10M |
|---|-----|----|-----|

