

**ANURAG Engineering College**

(An Autonomous Institution)

II B.Tech II Semester Supplementary Examinations, December-2024

**ANALOG ELECTRONIC CIRCUITS**

(ELECTRICAL AND ELECTRONIC ENGINEERING)

**Time: 3 Hours****Max. Marks: 75****Section – A (Short Answer type questions)****(25 Marks)****Answer All Questions**

Course Outcome	B.T Level	Marks
CO1	L1	2M
CO1	L2	3M
CO2	L1	2M
CO2	L2	3M
CO3	L1	2M
CO3	L2	3M
CO4	L1	2M
CO4	L2	3M
CO5	L1	2M
CO5	L2	3M

- Compare the current gains of CE, CB, & CC amplifiers?
- Write advantages of h-Parameters.
- What is Thermal Runaway?
- Discuss the importance of heat sinks?
- Define Clipper Circuit.
- List the applications of voltage comparator?
- Define storage time for transistor.
- Explain how transistor acts as a switch?
- Define Multivibrator?
- List and Explain types of Triggerings?

**Section B (Essay Questions)****Answer all questions, each question carries equal marks.****(5 X 10M = 50M)**

- |   |     |    |     |
|---|-----|----|-----|
| 11. A) Derive the expressions for $A_I$ , $A_V$ , $R_I$ , $R_O$ , $A_{V_S}$ & $A_{I_S}$ by using approximate analysis of the CE amplifiers?                   | CO1 | L3 | 10M |
| <b>OR</b>   |     |    |     |
| B) Draw the small signal equivalent of JFET CD amplifier and obtain its voltage gain, input impedance and output impedance.                                   | CO1 | L3 | 10M |
| 12. A) Demonstrate the principle operation of Class-A transformer coupled power amplifier and derive the efficiency?  | CO2 | L3 | 10M |
| <b>OR</b>   |     |    |     |
| B) With the help of a suitable circuit diagram, show that the maximum conversion efficiency of a class B power amplifier is 78.5%.                            | CO2 | L3 | 10M |
| 13. A) Analyze the typical circuit for clipping at two independent levels and draw the input & output waveforms, if the input signal is a sinusoidal voltage? | CO3 | L3 | 10M |
| <b>OR</b>   |     |    |     |
| B) State and Prove Clamping Circuit theorem. Draw and explain Positive clamping circuit and Negative clamping circuit.  | CO3 | L3 | 10M |
| 14. A) Explain the saturation parameters of transistor and their variation with temperature?  | CO4 | L3 | 10M |
| <b>OR</b>   |     |    |     |
| B) With the help of suitable waveforms of switching times of diode switch derive the expression for reverse recovery time.                                    | CO4 | L3 | 10M |
| 15. A) Explain the operation of fixed bias Bistable Multivibrator and derive the expression for stable state voltages and currents?                           | CO5 | L3 | 10M |
| <b>OR</b>   |     |    |     |
| B) Draw and Explain the working of Astable Multivibrator and explain Design procedure?  | CO5 | L3 | 10M |