

ANURAG Engineering College

(An Autonomous Institution)

I B.Tech I Semester Supplementary Examinations, June/July– 2024

**ELECTRICAL CIRCUITS
(COMMON TO EEE & ECE)**

Time: 3 Hours

Max. Marks: 75


Section – A (Short Answer type questions)

(25 Marks)

Answer All Questions

Course Outcome	B.T Level	Marks
CO1	L1	2M
CO1	L1	3M

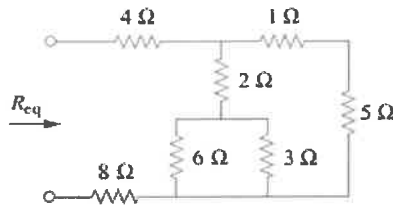1. What are the properties of an inductor and capacitor?
2. Find the Equivalent Resistance R_{eq} from the given circuit




- | | | | |
|---|-----|----|----|
| 3. What is MMF, Magnetic flux, Reluctance? | CO2 | L1 | 2M |
| 4. What is Composite magnetic circuit? What are the uses of Dot convention? | CO2 | L1 | 3M |
| 5. Define form factor of a periodic sine wave form. | CO3 | L1 | 2M |
| 6. Define reactance, impedance, susceptance and admittance | CO3 | L1 | 3M |
| 7. Draw the Locus diagram of series RC circuit with varying resistance R | CO4 | L1 | 2M |
| 8. Explain concept of bandwidth and quality factor | CO4 | L1 | 3M |
| 9. State Norton's theorem | CO5 | L1 | 2M |
| 10. State Maximum power transfer theorem | CO5 | L1 | 3M |

Section B (Essay Questions)

Answer all questions, each question carries equal marks.

(5 x 10M = 50M)


- | | | | |
|---|-----|----|-----|
| 11. A) A Pure Inductance Of 3mh Carries A Current Of The Waveform Shown in Fig. Solve and Sketch The Waveform Of V(t) | CO1 | L3 | 10M |
|---|-----|----|-----|

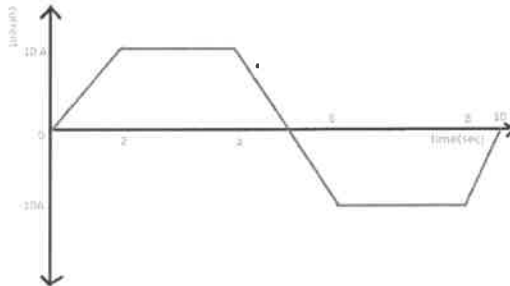

OR


B) i) Find the equivalent resistance across AB for the circuit shown in below Figure. Each resistance value is equal to 3Ω

CO1 L2 5M

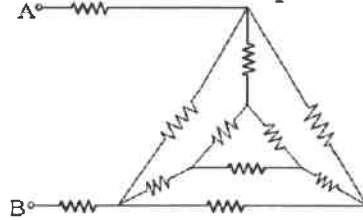

ii) Solve current i_1 , i_2 and i_3 from the given circuit using mesh analysis

CO1 L3 5M

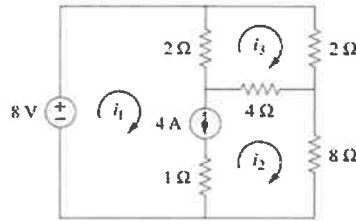


12. A) Explain the concept of self and mutual inductance. Relate coefficient of coupling and self, mutual inductance.

CO2 L2 10M

OR

B) What is a series magnetic circuit? Sketch the dotted equivalent circuit for the coupled coils shown in figure and find the current I?

CO2 L1 10M

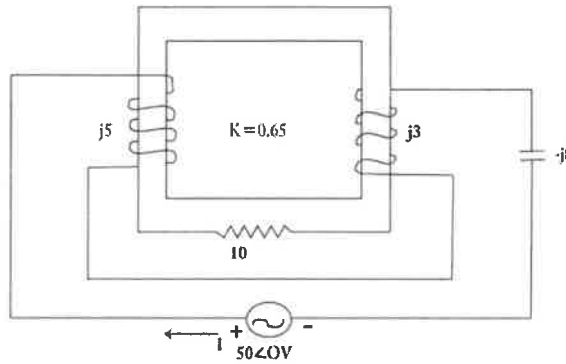


13. A) Explain the steady state analysis of RC parallel circuit with sinusoidal input

CO3 L2 10M

OR

B) i) Solve the average and rms value for the given waveform

CO3 L3 [5+5]M

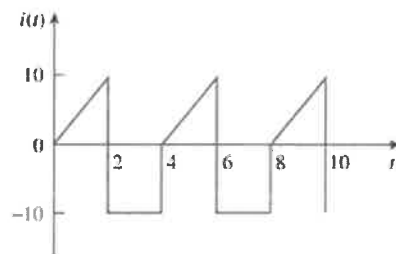


ii) The circuit, having two impedances of $Z_1 = (8 + j15)\Omega$ and $Z_2 = (6 - j8)\Omega$ in parallel, is connected to a single-phase ac supply and the current drawn is 10 A. Solve each branch current, both in magnitude and phase, and also the supply voltage.


14. A) Explain the Locus Diagram of parallel RC Circuit with varying Resistance 'R'. CO4 L2 10M

OR

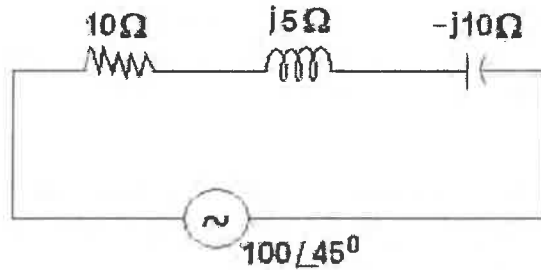B) The circuit shown in the figure. Solve (i) resonant frequency (ii) current at resonance (iii) voltage across L and C at resonance (iv) Q factor. CO4 L3 10M



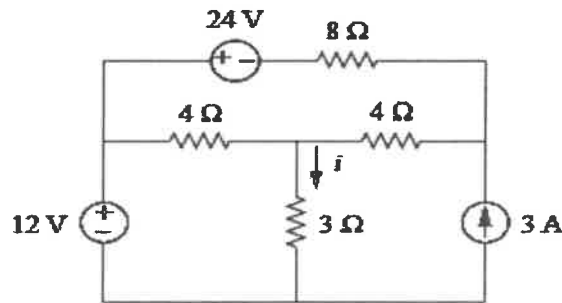15. A) For the circuit given below Figure, use superposition theorem to Solve current I flowing through 3Ω resistor. CO5 L3 10M



OR

B) State and Explain Milliman's Theorem. Find the current flowing (6+j8) Ω impedance using Milliman's Theorem CO5 L2 10M

