

ANURAG Engineering College

(An Autonomous Institution)

II B.Tech II Semester Supplementary Examinations, June/July-2024

BASIC ELECTRICAL & ELECTRONICS ENGINEERING

(CIVIL ENGINEERING)

Time: 3 Hours

Max. Marks: 75

Section – A (Short Answer type questions)

Answer All Questions

(25 Marks)

1. State the ohm's law.
2. Define resistance. What is V-I relation of resistance?
3. What is meant by Dynamically induced emf.
4. What are the various losses in a DC motor.
5. What is the purpose of using core in a transformer?
6. What are the different losses in a 3 –phase induction machine?
7. Distinguish between PNP and NPN transistor.
8. Give the detailed construction of Bridge rectifier.
9. State the magnetic deflection.
10. What are the various components of CRT?

Course Outcome	B.T Level	Marks
CO1	L1	2M
CO1	L1	3M
CO2	L2	2M
CO2	L2	3M
CO3	L2	2M
CO3	L2	3M
CO4	L1	2M
CO4	L1	3M
CO5	L2	2M
CO5	L2	3M

Section B (Essay Questions)

Answer all questions, each question carries equal marks.

(5 X 10M = 50M)

11. A) i) Give the detailed classification of independent sources.
 ii) For the circuit in Fig.1, find voltages V1 and V2.

CO1 L3 5M

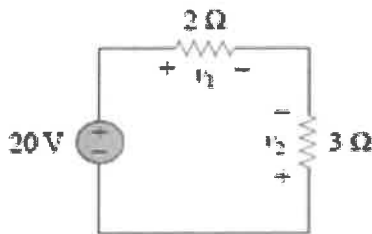


Fig.1.

5M

OR

- B) Obtain the node voltages 1 & 2 in the circuit in Fig.2

CO1 L3 10M

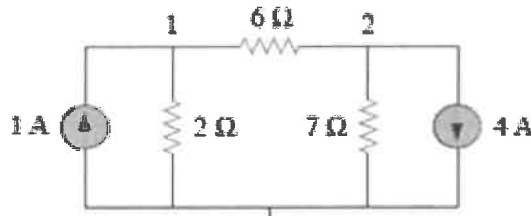


Fig.2.

12. A) i) Derive an expression for EMF equation of a DC generator.
 ii) List various losses in DC generator.

CO2 L3 5M

5M

OR

- B) i) Write the torque equation of DC motor and explain
 ii) Explain different characteristics of DC shunt motor.

CO2 L3 5M

5M

13. A) A 25 kVA , 2200/220 V, 50 Hz single phase transformer obtained the following test results,
 OC test (L.V side) = 220V, 12 A, 100 w
 SC test(H.V Side) = 100V, 7A, 310 w
 Calculate the parameters of the equivalent circuit of transformer referred to L.V side and draw the equivalent circuit.
- OR**
- B) i) Explain torque-slip characteristics of three phase induction motor.
 ii) Discuss various losses in three phase induction motor.
14. A) Draw the circuit diagram of a full bridge rectifier circuit and calculate
 i) I_{dc} ii) I_{rms} iii) ripple factor.
- OR**
- B) i) Sketch typical CB input characteristics curve for an NPN transistor.
 ii) How would you calculate the input dynamic resistance of the transistor?
15. A) i) Explain the block diagram of CRT.
 ii) Write short notes on Sensitivity and Deflection.
- OR**
- B) i) Derive the expression for magnetic deflection sensitivity of CRO.
 ii) Discuss how current and frequency are measured with CRO.