

**ANURAG Engineering College**

(An Autonomous Institution)

II B.Tech II Semester Supplementary Examinations, June/July-2024

**ANALOG ELECTRONIC CIRCUITS**

(ELECTRICAL AND ELECTRONICS ENGINEERING)

Time: 3 Hours

Max. Marks: 75

**Section – A (Short Answer type questions)****(25 Marks)****Answer All Questions**

- List out the benefits of h-parameter?
- Explain its impact on operational frequency.
- Compare the characteristics of large signal and small signal amplifiers
- What is the drawback of class B amplifier. How its overcome in class AB amplifier.
- List any 5 applications of clipper circuits.
- Why clamper circuit referred as DC restorer circuits?
- How the diode is acts as a switch?
- Illustrate the phenomenon of “latching” in a transistor switch.
- Define Multivibrator.
- Draw the hysteresis characteristics of the Schmitt trigger circuit and explain.

Course Outcome	B.T Level	Marks
CO1	L1	2M
CO1	L2	3M
CO2	L3	2M
CO2	L2	3M
CO3	L1	2M
CO3	L2	3M
CO4	L2	2M
CO4	L3	3M
CO5	L1	2M
CO5	L2	3M

**Section B (Essay Questions)****Answer all questions, each question carries equal marks.****(5 X 10M = 50M)**


11. A) Explain the high frequency analysis of BJT Amplifier. Define cut-off frequency, transition frequency and derive their values in terms of the circuit parameters.

CO1 L3 10M

**OR**

- B) Consider the common emitter BJT amplifier circuit. Assume  $V_{CC}=15V$ ,  $\beta=150$ ,  $V_{BE}=0.7V$ ,  $R_E=1K\Omega$ ,  $R_1=47K\Omega$ ,  $R_C=4.7K\Omega$ ,  $R_2=10K\Omega$ ,  $R_S=100\Omega$ ,  $R_L=47K\Omega$ .

CO1 L3 10M

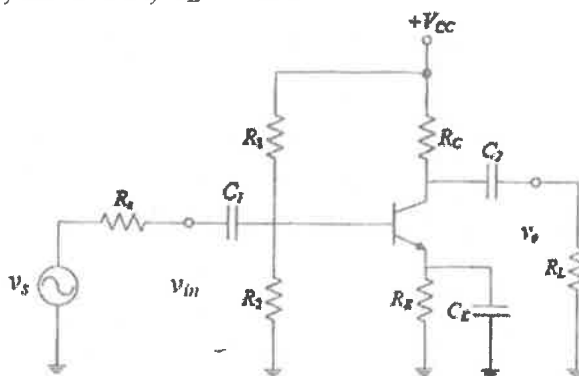Draw the equivalent circuit and determine  $R_{in}$ ,  $R_{out}$ ,  $A_v$ ,  $A_i$ .

12. A) With a neat diagram, explain the working of complementary Push Pull amplifier CO2 L2 10M
- OR**
- B) Explain the operation of transformer-coupled class A power amplifier and the need of heat sink in circuits. CO2 L2 10M
13. A) Explain with a neat diagram and waveforms explain the operation of different types of clampers. CO3 L2 10M
- OR**
- B) Illustrate the circuits of different types of clippers and explain their operation. CO3 L2 10M
14. A) Explain the terms pertaining to transistor switching characteristics. CO4 L2 10M  
 i) Rise time.  
 ii) Delay time.  
 iii) Turn-on time.  
 iv) Storage time.  
 v) Fall time.
- OR**
- B) Write Short notes on: CO4 L2 10M  
 i) Diode switching times  
 ii) Switching characteristics of transistors
15. A) Describe with neat circuit diagram and waveform of Bistable Multivibrator. CO5 L2 10M
- OR**
- B) Discuss the operation of collector coupled monostable multivibrator with its output waveforms. CO5 L2 10M