

**ANURAG Engineering College**

(An Autonomous Institution)

II B.Tech II Semester Supplementary Examinations, June/July – 2024

**SWITCHING THEORY AND LOGIC DESIGN**

(ELECTRICAL AND ELECTRONICS ENGINEERING)

**Time: 3 Hours****Max. Marks: 75****Section – A (Short Answer type questions)****(25 Marks)****Answer All Questions**

|   | Course Outcome | B.T Level | Marks |
|---|----------------|-----------|-------|
| 1. Find the decimal digits 0-9 in BCD code and 2 4 2 1 code.                | CO1            | L1        | 2M    |
| 2. Show that the dual of the Exclusive – OR is equal to its complement      | CO1            | L2        | 3M    |
| 3. Make use of the Boolean function $F(X,Y,Z)=\sum m(3,4,6,7)$ using K-map. | CO2            | L1        | 2M    |
| 4. Define a MUX and show how a MUX may be used as a sequence data selector. | CO2            | L2        | 3M    |
| 5. Compare Latch and Flip-Flop.   | CO3            | L1        | 2M    |
| 6. Define Level trigger, Edge trigger, Clock skew.                          | CO3            | L2        | 3M    |
| 7. Compare asynchronous and synchronous counters.                           | CO4            | L1        | 2M    |
| 8. What are the drawbacks of ripple counters.                               | CO4            | L2        | 3M    |
| 9. List the capabilities of finite state machine.                           | CO5            | L1        | 2M    |
| 10. Explain about partition techniques.                                     | CO5            | L2        | 3M    |

**Section B (Essay Questions)****Answer all questions, each question carries equal marks.****(5 X 10M = 50M)**

|  |     |    |     |
|--|-----|----|-----|
| 11. A) What is a reflected code? Write about reflected codes by giving examples.   | CO1 | L2 | 10M |
| <b>OR</b>  |     |    |     |
| B) Construct BCD code to Gray code converter with diagram.   | CO1 | L3 | 10M |
| 12. A) Simplified expressions in sum of products for the following Boolean functions using Karnaugh-Map.<br>i) $F(A, B,C,D) = \Sigma (7,13, 14, 15)$<br>ii) $F(w,x,y,z) = \Sigma (2,3,12,13,14,15)$  | CO2 | L2 | 10M |
| <b>OR</b>  |     |    |     |
| B) Simplify the following function using Tabular method $f(w,x,y,z)=\sum m(4,5,6,7,12,13,14)+\sum d(1,9,11,15)$  | CO2 | L3 | 10M |
| 13. A) Realize D-FF and T-FF using JK-FF. Draw the logic diagrams with their truth tables.   | CO3 | L2 | 10M |
| <b>OR</b>  |     |    |     |
| B) Write the conversion procedures of the flip-flops. Convert T-flip-flop to JK- flip-flop.  | CO3 | L2 | 10M |
| 14. A) Construct the state diagram for a two input, two output sequential circuit which is to produce an output $z=1$ with occurrence of an input 1 following a string of two or three consecutive input 0's. At all other times the output is to be 0, realize using JK flipflop. | CO4 | L3 | 10M |
| <b>OR</b>  |     |    |     |
| B) Develop and explain a synchronous MOD-12 down-counter using J-K flipflop.   | CO4 | L2 | 10M |

15. A) Explain the procedure of state minimization using the partition technique. CO5 L3 10M

**OR**

B) Analyze the ASM chart for Binary multiplier with an example. CO5 L3 10M