

ANURAG Engineering College
(An Autonomous Institution)

I B.Tech. I Semester Regular/Supplementary Examinations, Jan/Feb-2024

BASIC ELECTRICAL ENGINEERING
(COMMON TO CSE & AIML)

Time: 3 Hours

Max. Marks: 60

Section – A (Short Answer type questions)

(10 Marks)

Answer All Questions

	Course Outcome	B.T Level	Marks
1. List the Active Elements and Passive Elements.	CO1	L1	1M
2. State Norton's theorem	CO1	L1	1M
3. Define Admittance and impedance	CO2		1M
4. An alternating current is expressed as $I = 14.14 \sin 314t$. Determine. Instantaneous current when $t = 0.02\text{msec}$.	CO2	L1	1M
5. Enumerate the various losses associated with transformer	CO3	L1	1M
6. Write the expression for transformer ratio in terms voltage, current and turns	CO3	L2	1M
7. Define Slip of an Induction Motor?	CO4	L2	1M
8. State Faradays laws of electromagnetic induction	CO4	L2	1M
9. What is the importance of power factor?	CO5	L1	1M
10. What is the difference between wire & cable?	CO5	L1	1M


Section B (Essay Questions)

Answer all questions, each question carries equal marks.

(5 X 10M = 50M)

11. A) i) Determine the current in Branch A-B (across 20Ω) by

CO1 L3 5M

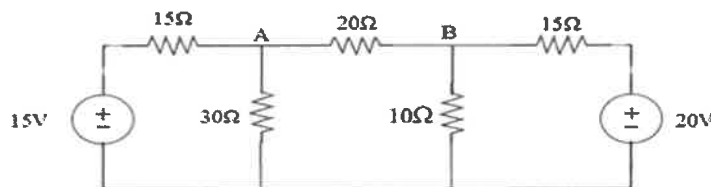

ii) State and explain Kirchoff's laws?

5M

OR

B) State and prove superposition theorem with suitable example.

CO1 L3 10M

12. A) i) Derive an expression for RMS values of sine wave form.

CO2 L2 5M

ii) Explain the power factor, apparent power, active power and reactive power

5M

OR

B) Derive an expression for the current and impedance for a series RL and RC circuit excited by a Sinusoidally alternating voltage. Draw the phasor diagrams.

CO2 L3 10M

13. A) i) A 2,200/200-V transformer draws a no-load primary current of 0.6 A and absorbs 400 watts. Find the magnetising and iron loss currents.

CO3 L3 5M

ii) Derive the condition for maximum efficiency of a transformer

5M

OR

B) Draw the constructional diagram of a single-phase transformer and explain all the parts.

CO3 L2 10M

14. A) i) Explain working Principle Single Phase Induction motor. CO4 L3 5M
ii) Draw and explain about the characteristics of a DC shunt motor. 5M
- OR**
- B) Explain the Generation of rotating magnetic field in three phase Induction motor with necessary diagrams? CO4 L2 10M
15. A) i) What is Fuse & explain the principle of operation of Fuse. CO5 L2 5M
ii) Explain about different types of circuit breakers. 5M
- OR**
- B) With neat diagrams, explain various types of fuses used in electrical wiring systems CO5 L2 10M