

ANURAG Engineering College

(An Autonomous Institution)

I B.Tech II Semester Supplementary Examinations, Jan/Feb-2024

ELECTRONIC DEVICES AND CIRCUITS

(COMMON TO ECE, CSE, IT & AI&ML)

Time: 3 Hours**Max. Marks: 60****Section – A (Short Answer type questions)****(10 Marks)****Answer All Questions**

	Course Outcome	B.T Level	Marks
1. Define Reverse Saturation Current in PN Junction Diode.	CO1	L1	1M
2. Draw the equivalent circuits of PN diode.	CO1	L2	1M
3. What is ripple factor? And mention typical value for Half Wave Rectifier.	CO2	L1	1M
4. State Clamping Circuit Theorem.	CO2	L1	1M
5. Explain the operation of BJT.	CO3	L2	1M
6. Give the relation between α , β , and γ	CO3	L2	1M
7. Write the differences between JFET and BJT.	CO4	L2	1M
8. Why we call FET as a Voltage Controlled Device?	CO4	L1	1M
9. What are the applications of UJT?	CO5	L2	1M
10. What is tunnelling?	CO5	L1	1M

Section B (Essay Questions)**Answer all questions, each question carries equal marks.****(5 X 10M = 50M)**

11. A) Derive the expression for transition capacitance of a P-N junction Diode.	CO1	L3	10M
OR			
B) How a diode is used as switch and defines all switching times.	CO1	L3	10M
12. A) Draw and explain Bridge Rectifier with the help of wave forms and derive the following parameters. i) V_{DC} ii) Efficiency iii) Ripple Factor iv) TUF .	CO2	L3	10M
OR			
B) Explain the operation of positive clamping and negative clamping circuits.	CO2	L3	10M
13. A) Draw and explain the input and output characteristics of BJT for CB configuration.	CO3	L3	10M
OR			
B) i). A transistor has a typical β of 100. If the collector current is 40mA, what is the value of emitter current? ii). Explain the working of the transistor as a switch.	CO3	L3	5M
	CO3		5M
14. A) Explain the construction, principle of operation and Volt-Ampere characteristics of JFET.	CO4	L3	10M
OR			
B) Explain with the help of neat diagrams, the structure and working principles of a N-channel enhancement mode MOSFET.	CO4	L3	10M
15. A) Draw the circuit diagram of SCR and explain its operation along with its characteristics.	CO5	L3	10M
OR			
B) Explain V-I characteristics of Zener diode with neat diagram.	CO5	L3	10M

