

ANURAG Engineering College

(An Autonomous Institution)

I B.Tech II Semester Regular/Supplementary Examinations, June/July – 2024

BASIC ELECTRICAL ENGINEERING

(COMMON TO ECE & IT)

Time: 3 Hours

Max. Marks: 60

Section – A (Short Answer type questions)

(10 X 1M = 10M)

Answer All Questions

Course Out come	B.T Level	Marks
CO1	L2	1M
CO1	L2	1M
CO2	L2	1M
CO2	L2	1M
CO3	L2	1M
CO3	L1	1M
CO4	L2	1M
CO4	L2	1M
CO5	L1	1M
CO5	L1	1M

1. State Ohm's law.
2. State KCL.
3. Define RMS value of alternating current.
4. Define Peak factor.
5. Define Voltage Regulation of transformer.
6. Mention the various losses which occur in a transformer.
7. State Flemming's Right Hand rule.
8. Define Slip.
9. What are the components of LT switchgear.
10. What is the necessity of Earthing?


Section B (Essay Questions)

Answer all questions, each question carries equal marks.

(5 X 10M = 50M)

11. A) i) Explain in detail about Thevenin's Theorem.
 ii) Find the current flowing through the $1\ \Omega$ resistor using Thevenin's theorem


CO1	L3	5M
		5M

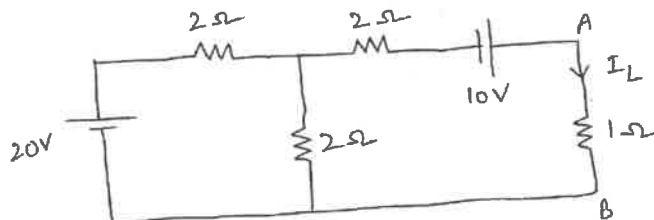

OR

- B) i) Explain in detail about Superposition Theorem.
 ii) Find the current I in the circuit using Superposition theorem

CO1	L3	5M
		5M

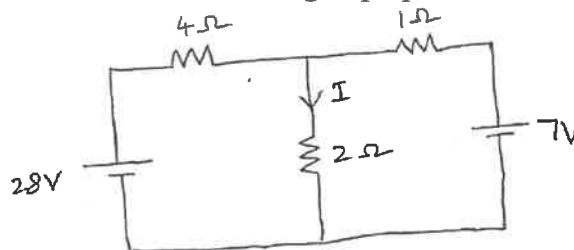

12. A) i) Explain about Real power and reactive power
 ii) A resistance of 10 ohms, inductance of 0.5H, capacitance of $10\ \mu\text{F}$ are connected in series across 50V, 50Hz supply, calculate impedance, current, p.f, power consumed.

CO2	L3	5M
		5M

OR

- | | | | | |
|-----------|---|-----|----|----------|
| B) | What are three phase balanced circuits, derive voltage and current relations in star and delta connections. | CO2 | L3 | 10M |
| 13. A) | i) Explain the working of single phase transformer
ii) Distinguish between Ideal and Practical transformer and draw the equivalent circuits of ideal and practical transformers. | CO3 | L3 | 5M
5M |
| OR | | | | |
| B) | A 3 KVA , single phase, 50 Hz, 230/115 V transformer gave the following test results
OC test: 115 V, 0.6 A, 10 W
SC test: 60 V, 13 A, 200 W
If the power factor of the load is 0.8 lagging, Calculate the
i) efficiency at full-load and ii) efficiency at half full-load | CO3 | L3 | 10M |
| 14. A) | i) Draw the performance characteristics of dc generators
ii) Draw the performance characteristics of dc motors | CO4 | L3 | 5M
5M |
| OR | | | | |
| B) | i) Explain the generation of rotating magnetic field.
ii) Explain the construction and working of a three-phase induction motor | CO4 | L3 | 5M
5M |
| 15. A) | What are the types of Batteries and explain their characteristics. | CO5 | L3 | 10M |
| OR | | | | |
| B) | i) Explain the elementary calculations for energy consumption.
ii) What do you understand by power factor? Explain the necessity of improving power factor? | CO5 | L3 | 5M
5M |