

ANURAG Engineering College

(An Autonomous Institution)

II B.Tech. I Semester Regular Examinations, Jan/Feb-2024

DIGITAL ELECTRONICS**(COMMON TO CSE & IT)****Time: 3 Hours****Max. Marks: 60****Section – A (Short Answer type questions)****(10 Marks)****Answer All Questions**


	Course Outcome	B.T Level	Marks
1. Apply De-Morgan's theorem to simplify $(A+BC)'$.	CO1	L2	1M
2. Convert $(115)_{10}$ and $(235)_{10}$ into hexadecimal numbers.	CO1	L1	1M
3. Show how to connect NAND gates to get an AND gate and OR gate?	CO2	L2	1M
4. Mention the significance of minimization techniques	CO2	L1	1M
5. Design Half – adder using only NAND gates.	CO3	L2	1M
6. Design a 2:1 Multiplexer	CO3	L1	1M
7. List the differences between Asynchronous and Synchronous circuits	CO4	L1	1M
8. Realize T Flip Flop using SR Flip Flop	CO4	L2	1M
9. Compare and contrast static RAM and dynamic RAM	CO5	L2	1M
10. What is PLD? List their types	CO5	L1	1M

Section B (Essay Questions)**Answer all questions, each question carries equal marks.****(5 X 10M = 50M)**

11. A) Convert $(73889.22)_{10}$ into the following number system.
 i) Binary number, Octal number, Hexadecimal number
 ii) Subtract $(111001)_2$ from (101011) using 1's complement?
OR
- B) i). Simplify the following expression: $Y = (A + B)(A + C')(B' + C')$
 ii). Prove that $ABC + ABC' + AB'C + A'BC = AB + BC + CA$
12. A) i) Design the circuit by Using NAND gates $F = ABC' + DE + AB'D'$
 ii) Simplify and implementation the following SOP function using NOR gates $F(A,B,C,D) = \sum m(0,1,4,5,10,11,14,15)$
OR
- B) Reduce the expression $f(x,y,z,w) = \pi M(0,2,7,8,9,10,11,15)$.d (3,4) using K-Map
13. A) i) Design a full adder.
 ii) Design a full subtractor
OR
- B) Design a 4-bit Magnitude comparator with the three outputs
 $A=B$, $A<B$, $A>B$

14. A) Design a clocked synchronous sequential logic circuit using JK flip flops for the following state diagram. Use state reduction if possible.

CO4 L3 10M

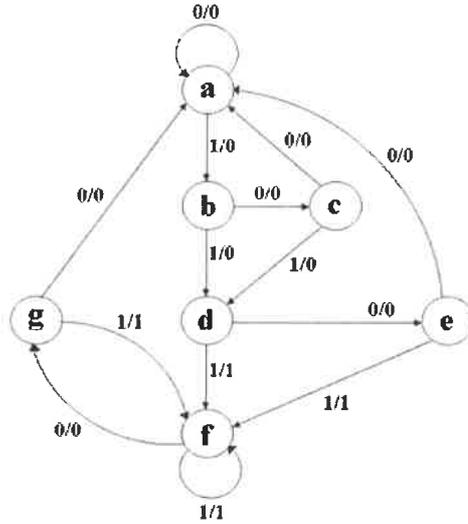

OR

B) Design a synchronous counter with states 0, 1, 2, 3, 0, 1, ... using JK flip flop

CO4 L3 10M

15. A) Give the classification of semiconductor memories

CO5 L2 10M

OR

B) A combinational circuit is defined as the function $F1 = AB'C' + AB'C + ABC$ and $F2 = A'BC + AB'C + ABC$. Implement the digital circuit with a PLA having 3 inputs, 3 product terms and 2 outputs

CO5 L2 10M