

**ANURAG Engineering College**

(An Autonomous Institution)

II B.Tech. I Semester Regular Examinations, Jan/Feb-2024

**NETWORK ANALYSIS AND SYNTHESIS**

**(ELECTRONICS AND COMMUNICATION ENGINEERING)**

**Time: 3 Hours**

**Max. Marks: 60**

**Section – A (Short Answer type questions)**

**(10 Marks)**

**Answer All Questions**

1. What is dot convention?
2. What is a cut set?
3. Define Steady state.
4. Define Quality factor. and bandwidth
5. List different types of attenuators
6. What is the Condition for symmetric and reciprocity of h-parameters?
7. What Is a Filter?
8. What is a constant K low pass filter?
9. What are poles and zeros?
10. What are the disadvantages of transfer function?

Course Outcome	B.T Level	Marks
CO1	L1	1M
CO1	L1	1M
CO2	L1	1M
CO2	L1	1M
CO3	L1	1M
CO3	L1	1M
CO4	L1	1M
CO4	L1	1M
CO5	L1	1M
CO5	L1	1M

**Section B (Essay Questions)**

**Answer all questions, each question carries equal marks.**

**(5 X 10M = 50M)**

11. Derive an expression for coefficient of coupling between two mutually coupled coils.

CO1	L2	10M
-----	----	-----

**OR**

- B) Explain the following: i) sub graph ii) connected graph iii) Planar graph.

CO1	L2	10M
-----	----	-----

12. Explain the DC response for a series RL circuit.

CO2	L2	10M
-----	----	-----

**OR**

- B) Show that the resonant frequency is the geometric mean of two half power frequencies

CO2	L2	10M
-----	----	-----

13. For the two-port network shown in figure 1, find the short-circuit admittance parameter.

CO3	L3	10M
-----	----	-----

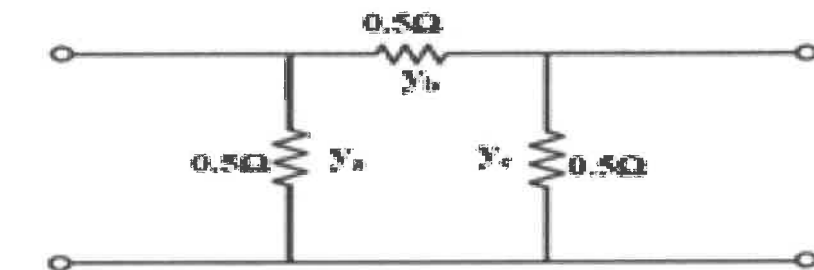


Figure 1

**OR**

- B) Explain the concept of poles, zeros, their significance and necessary conditions for driving point functions and transfer functions?

CO3	L2	10M
-----	----	-----

14. Design a constant K high pass filter and explain its design procedure in detail. CO4 L3 10M

OR

B) Design the m-derived high pass filter. CO4 L3 10M

15. Obtain the first form of the Foster Network for the driving point impedance of LC network given as:  
A)

$$Z(s) = 10(s^2+4)(s^2+16) / s(s^2+9)$$

CO5 L3 10M

OR

B) Find the R-L representation by Foster 1<sup>st</sup> of the impedance function:-

$$Z(s) = \frac{2(s+1)(s+3)}{(s+2)(s+6)}$$

CO5 L3 10M