

ANURAG Engineering College

(An Autonomous Institution)


II B.Tech I Semester Supplementary Examinations, June/July – 2024

NETWORK ANALYSIS AND SYNTHESIS**(ELECTRONICS AND COMMUNICATION ENGINEERING)****Time: 3 Hours****Max. Marks: 60****Section – A (Short Answer type questions)****(10 Marks)****Answer All Questions**

	Course Outcome	B.T Level	Marks
1. Define the Mutual-inductance of magnetic circuit.	CO1	L1	1M
2. Define the terms trees and links for network graph theory.	CO1	L1	1M
3. Define the quality factor of resonance circuit.	CO2	L1	1M
4. Write the differences between series and parallel resonance	CO2	L1	1M
5. Why ABCD-parameter are called as transmission line parameters?	CO3	L2	1M
6. What is a two port network?	CO3	L1	1M
7. Define the lattice section?	CO4	L1	1M
8. When lattice section can be called as Symmetrical or Asymmetrical lattice	CO4	L2	1M
9. Define the transfer impedance and admittance.	CO5	L1	1M
10. Differentiate between network analysis and network synthesis.	CO5	L2	1M

Section B (Essay Questions)**Answer all questions, each question carries equal marks.****(5 X 10M = 50M)**

11. A) i) Two coils having self-inductances of 4mH and 7mH respectively are connected in parallel. If the mutual inductance between them is 5mH, find the equivalent inductance.
ii) Explain the condition for ideal transformer.
- OR**
- B) i) Explain the dot convention rule for coupled circuit.
ii) What is coupling coefficient? Derive the expression for it
12. A) Determine whether the RLC series circuit shown in Fig. Under damped, over damped or critically damped. Also find $V_L(0^+)$, di/dt and $i(\infty)$.

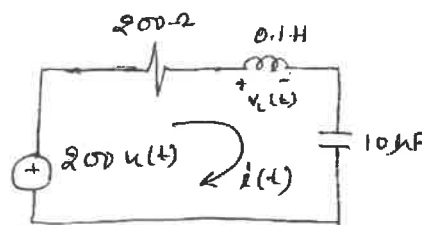**OR**

- B) i) Derive the step response of RL circuit in s-domain.
ii) A series connected circuit has $R = 4 \Omega$ and $L = 25 \text{ mH}$.
a) Calculate the value of C that will produce a quality factor of 50.
b) Find ω_1 , ω_2 and bandwidth.

13. A) A two port network has the Z-parameter $Z_{11} = 200 \Omega$, $Z_{22} = 30 \Omega$ and $Z_{12} = Z_{21} = 40 \Omega$ then find the ABCD parameter and h-parameter. CO3 L3 10M

OR


B) Explain about the parameters used for series connected two port network. CO3 L3 10M

14. A) Explain the classification of pass band and stop band Filter. CO4 L3 10M

OR

B) Find the cut-off frequency for an RC low pass filter of $R = 8.2 \Omega$ and $0.0033 \mu\text{F}$. CO4 L2 10M

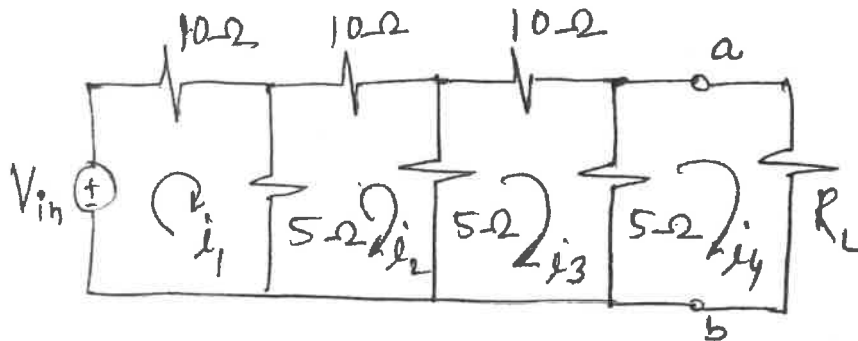15. A) For the ladder network of the figure, obtain the transfer resistance as expressed by the ratio of V_{in} to i_4 . CO5 L3 10M



OR

B) Two circuit, the impedance are which given by $Z_1 = (4 + j3) \Omega$ and $Z_2 = (8 - j6) \Omega$ are connected in parallel. If the total current supplied is 15A, what is the value of total admittance of the circuit? CO5 L3 10M