

Model Question Paper
ANURAG Engineering College
 (An Autonomous Institution)
 III B.Tech. II Semester Regular Examinations, June -2025
POWER SEMICONDUCTOR DRIVES
(ELECTRICAL AND ELECTRONICS ENGINEERING)

Time: 3 Hours

Max.Marks:60

| Section – A (Short Answer type questions) | | (10 Marks) | | |
|--|---|----------------|-----------|----------------|
| Answer All Questions | | Course Outcome | B.T Level | Marks |
| 1. | Define electric drive? | CO1 | L1 | 1M |
| 2. | Mention various types of power converters? | CO1 | L2 | 1M |
| 3. | Write any two differences between mechanical and electrical braking? | CO2 | L1 | 1M |
| 4. | What are the different types of control strategies in a D.C chopper? | CO2 | L1 | 1M |
| 5. | What is meant by V/F control? | CO3 | L2 | 1M |
| 6. | Differentiate VSI and CSI? | CO3 | L2 | 1M |
| 7. | Name the rotor resistance control methods in induction motor? | CO4 | L1 | 1M |
| 8. | What are the advantages of static Kramer drive? | CO4 | L2 | 1M |
| 9. | What are different modes employed to obtain variable frequency control of synchronous motor drive? | CO5 | L2 | 1M |
| 10. | What is load commutation? | CO5 | L1 | 1M |
| Section B (Essay Questions) | | | | |
| Answer all questions, each question carries equal marks. | | (5 X10M = 50M) | | |
| 11. | Explain Single Phase fully controlled converter fed d.c separately excited motor and draw the output voltage and current wave forms, Speed and Torque expressions | CO1 | L3 | 10M |
| OR | | | | |
| 12. | Explain Three Phase semi controlled converters connected to d.c separately excited motor and draw the output voltage current wave forms, Speed and Torque expressions, Speed – Torque characteristics | CO1 | L3 | 10M |
| 13. | Explain about the following electric braking methods. i) Regenerative braking ii) Dynamic or rheostatic braking iii) Plugging | CO2 | L2 | 4M 3M 3M |
| OR | | | | |
| 14. | A 220V, 24A, 1000rpm, separately excited DC motor having an armature resistance of 2Ω is controlled by a chopper. The chopping frequency is 500Hz and the input voltage is 230V. Calculate the duty ratio for a motor torque of 1.2 times rated torque at 500rpm | CO2 | L3 | 10M |
| 15. | Draw a block schematic diagram for automatic speed control of three phase case induction motor using solid state AC voltage controller on starter side. | CO3 | L3 | 10M |

| OR | | | | |
|------------|---|-----|----|-----|
| 16. | Explain with suitable block diagrams the various types of VSI-controlled Induction motor drive? | CO3 | L2 | 10M |
| OR | | | | |
| 17. | Explain briefly about the static scherbius system for speed control of slip ring induction motor drive? | CO4 | L3 | 10M |
| OR | | | | |
| 18. | Draw and explain a closed loop operation for a static Kramer controlled drive? | CO4 | L3 | 10M |
| OR | | | | |
| 19. | Describe the open loop method of speed control of synchronous motor drive. | CO5 | L3 | 10M |
| OR | | | | |
| 20. | Describe separate controlled mode and self controlled mode of operation of a synchronous motor drive in detail and compare them | CO5 | L3 | 10M |